

## D.C. MOTOR CHARACTERISTICS

### Objective:

To study the load characteristics of D.C shunt & compound motors.

### Procedure:

#### **a. D. C. Shunt Motor:**

Connect as in FIG.1 (a). The armature resistance  $R_a$  is kept at its maximum position and  $R_{f1}$  at its zero position. SW1 is closed.  $R_a$  is cut out step by step completely.  $R_{f1}$  is adjusted so that the speed on no load is the rated speed. This field current is termed as  $I_{f0}$  and is kept constant throughout the experiment. Load is applied on the motor through the generator step by step by adjusting  $R_{f2}$  and the load resistance  $L$ . Note down  $V_t$ ,  $I_a$ ,  $T$  and  $N$ , checking each time that the field is constant at  $I_{f0}$ , where  $T$  is the torque read on the torque meter, and  $N$  is the speed in R.P.M read by the tachometer.

#### **b. D.C Compound Motor**

Cumulative operation is obtained when the direction of current through the series field is so as to aid the shunt field; differential operation is obtained when the series field opposes the shunt field. The series field is across S1-S2. The experiment is done for both differential and cumulative operation.

- i) The machine is connected as in FIG.1 (b). The motor is started as before and  $R_{f1}$  is adjusted so that the speed on no load is the rated speed;  $I_{f0}$  is kept constant as before at the value in Section 'a' above Switch SW2 is then closed and the load applied to the motor in steps by adjusting  $R_{f2}$  and the loading resistor  $L$ . Note down  $V_t$ ,  $T$ , and  $N$  each time checking that  $I_{f0}$  is constant.
- ii) If the connections in FIG 1 (b) give cumulative operation, reversal of S1-S2 will give differential operation, and vice versa. The experiment is carried out for both the operations. The motor may tend to race up during differential operation, so care should be taken not to exceed the rated current and to apply the load slowly in steps.

### Report:

$\omega = 2\pi N/60 =$  angular velocity

Express torque  $T$  in N-m.

1. Plot  $\omega$  ( Y-axis) against  $I_a$  for Tests I & II.
2. Plot  $T$  (Y-axis) against  $I_a$  for Tests I & II.
3. Plot  $\omega$  (Y-axis) against  $T$  for Tests I & II.
4. Write down or derive the equations relating  $\omega$ - $I_a$ ,  $T$ - $I_a$  and  $\omega$ -  $T$  for shunt, cumulative compound and differential compound operations. Justify the shapes of the curves obtained in each case.


### Observations:

Same tables for all cases.

- I. Shunt Motor
- II. Compound Motor (Cumulative)
- III. Compound Motor (Differential)

$I_{f0}$  = Amp. (Constant)

S.No.	$V_t$	$I_a$	N	T

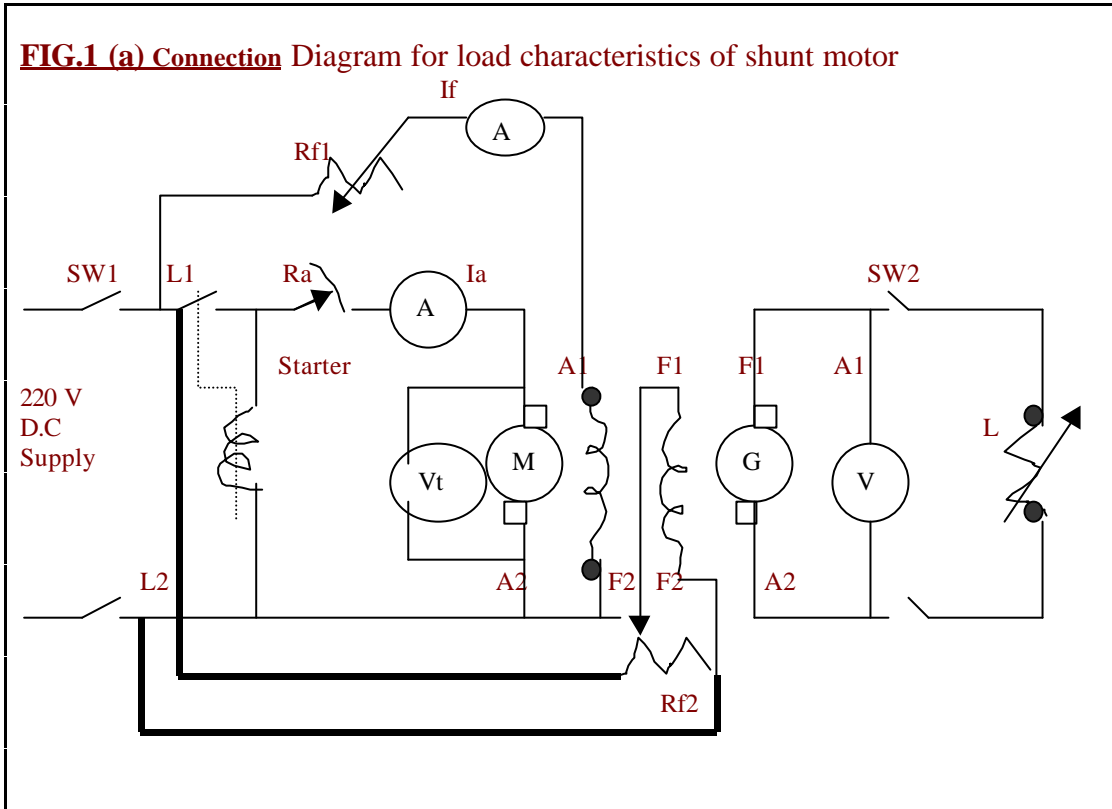

**FIG.1 (b)** Connection Diagram for load characteristics of compound motor

